



CAS

IEEE CIRCUITS AND SYSTEMS SOCIETY

UNIC-CASS

Mock Tapeout

“250 MHz *Quadrature Delay Locked Loop*”

27.01.2026



Content

1. **Fundamentals**
2. **QDLL Project:** Block Diagram and Specifications
3. **Schematics:** TOP and Sub-blocks: Symbols & Schematics & Layouts
4. **Characterization Testbenches**
5. **TOP Simulation:** Testbench with the IO-Cells. Characterization Testbenches.
6. **QDLL Layout:** Top Layout and layout within the pad ring.
7. **QDLL:** Pins and IO Cells.
8. **Project Status**

1- QDLL Fundamentals


1 - QDLL Fundamentals

The **Quadrature Delay Locked Loop (QDLL)** is a phase control system designed to delay a differential CMOS input signal by 90° , generating a differential quadrature-phase output.


The QDLL operates through three key components:

 1. **Phase Detector (PD) + Charge Pump (CP)**:: Measures the phase difference between the input signal ϕ_{in} and the delayed output ϕ_{out} , and generates a proportional voltage V_{cont} .
2. **Large Voltage-Controlled Delay Line (Large VCDL)**: Introduces a controllable delay to the input signal, adjusted by the control voltage V_{cont} .
3. **Feedback Loop**: Processes the phase error signal from the phase detector and adapts the VCDL delay until the phase difference is locked at 90° .

The main goal of the QDLL is to achieve and maintain a quadrature (90°) phase shift between the input and output signals.



QDLL block diagram

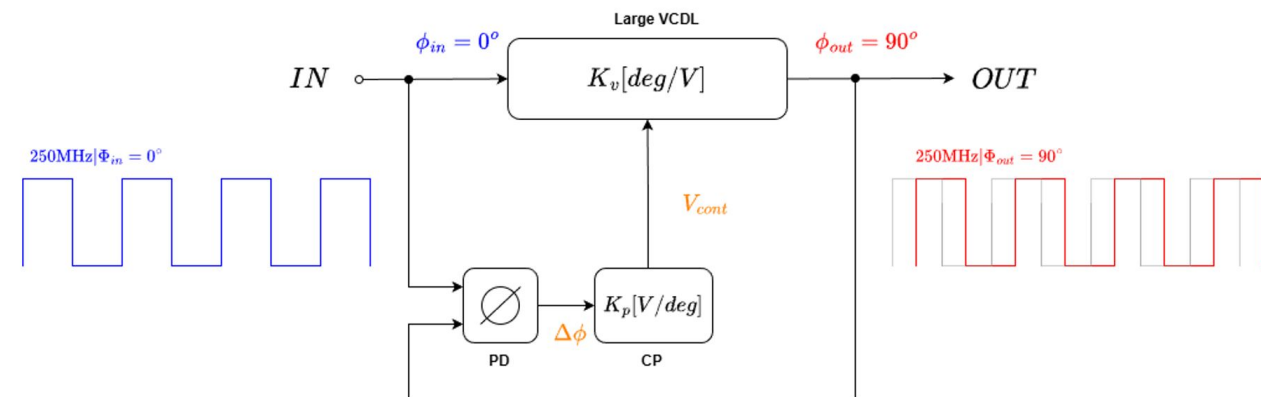

Single QDLL Operation

1 - QDLL Fundamentals


If we model the diagram of the single QDLL operation, we observe the phase detector compares the input and output phases (ϕ_{in} & ϕ_{out}), and any phase error is converted into a control voltage via the charge pump or loop filter. This voltage, V_{cont} , tunes the delay element (Large VCDL) with gain $K_v K_p$, adjusting the phase of the output signal ϕ_{out} .

On the other hand, using a single pole ($1/S$) in the feedback path guarantees inherent stability and ensures smooth convergence. Therefore, a simple RC network can be an effective choice for implementation.


This feedback mechanism ensures that the system locks the output phase at a fixed offset (e.g., 90° for QDLL) from the input phase eliminating steady-state phase error.

The Phase Converge plot shows that:

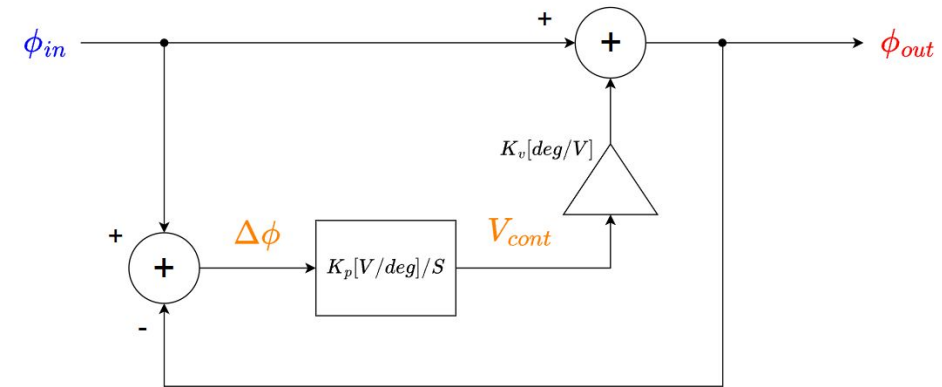- A stable locking point exists where the two characteristics intersect. (90° is the desired)
- The negative slope of the VCDL ensures that the loop has a stable operating point.



QDLL System Operation

 


Phase Convergence

2- QDLL Project Diagram & Specifications

2 - QDLL Project Diagram

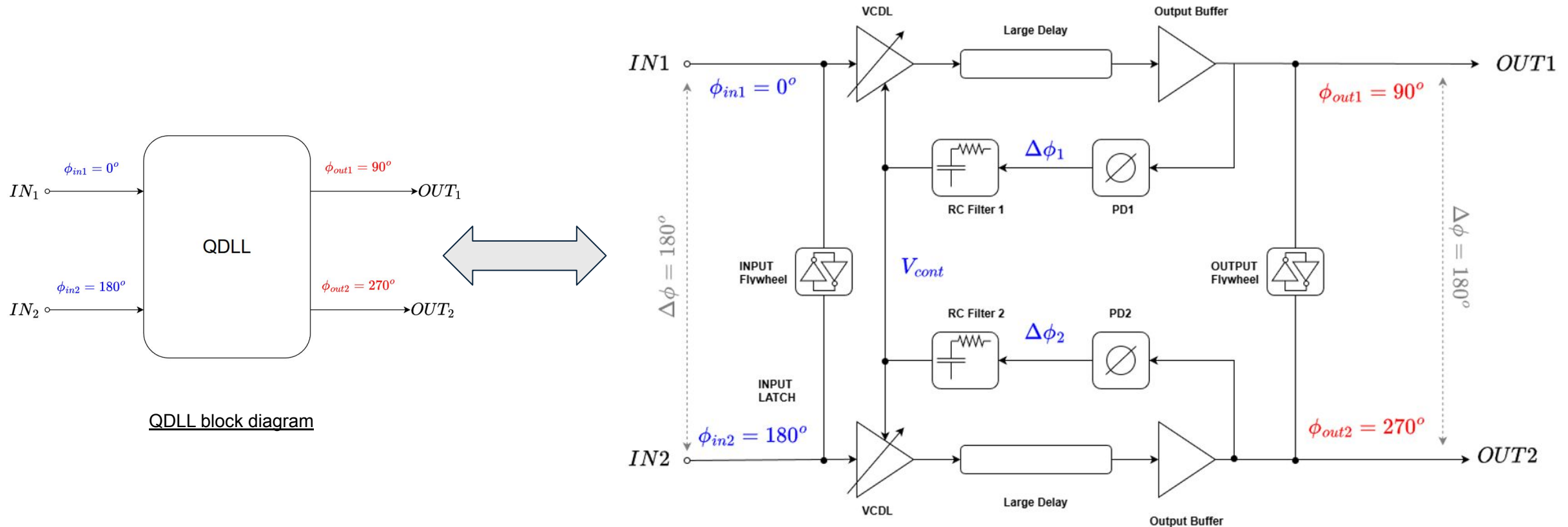For this project, two single-ended DLLs with differential outputs are used to generate two differential signals with 90° and 270° phase shifts. The RC filters and the large VCDLs are designed to stabilize each branch at a $90^\circ \pm 5^\circ$ phase difference at **250 MHz**. To ensure synchronization between the signal pairs, flywheel cells are added.



2 - QDLL Project Specifications

The design specifications were modified due to the high-frequency behavior of the I/O cells. As a result, the performance requirements were relaxed, along with adjustments to the project focus and the number of input/output pins.

Pins:

- 2 Bi-directional: VDD, VSS
- 2 inputs: inpad1, inpad2
- 2 outputs: outpad1, outpad2

Estimated Number of Pins:*

Input: *

2

Output: *

2

Bidirectional: *

2

Design Type:**

Analog




ihp 130 nm

QDLL Specifications	
Boundary Conditions	Requirement
Techn.	CMOS
Node	130 nm
Supply Voltage	$1.2 \pm 5\% \text{ V}$
Temperature	$[0, 65, 125] \text{ }^{\circ}\text{C}$
Input Amplitude	$[0, 1.2] \text{ V (CMOS)}$
Input Frequency	$250 \pm 25 \text{ MHz}$
Input/Output Type	Fully Differential
Specifications	Value
Phase Difference	$90 \pm 5 \text{ degrees}$
Output Swing	$[0, 1.2] \text{ V (CMOS)}$
t _{rise} /t _{fall} output	<
Vcont_ripple	$\geq 9 \text{ bits}$
Output Jitter	$\geq 7.5 \text{ bits}$


3- QDLL Project Schematics & Layouts

3 - QDLL Schematics (TOP)

- Differential QDLL TOP:

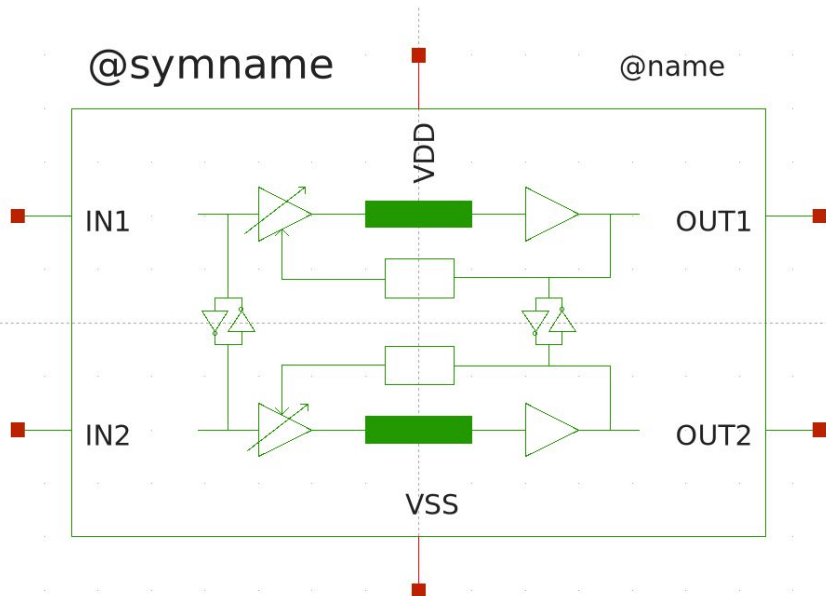

QDLL_TOP.sym

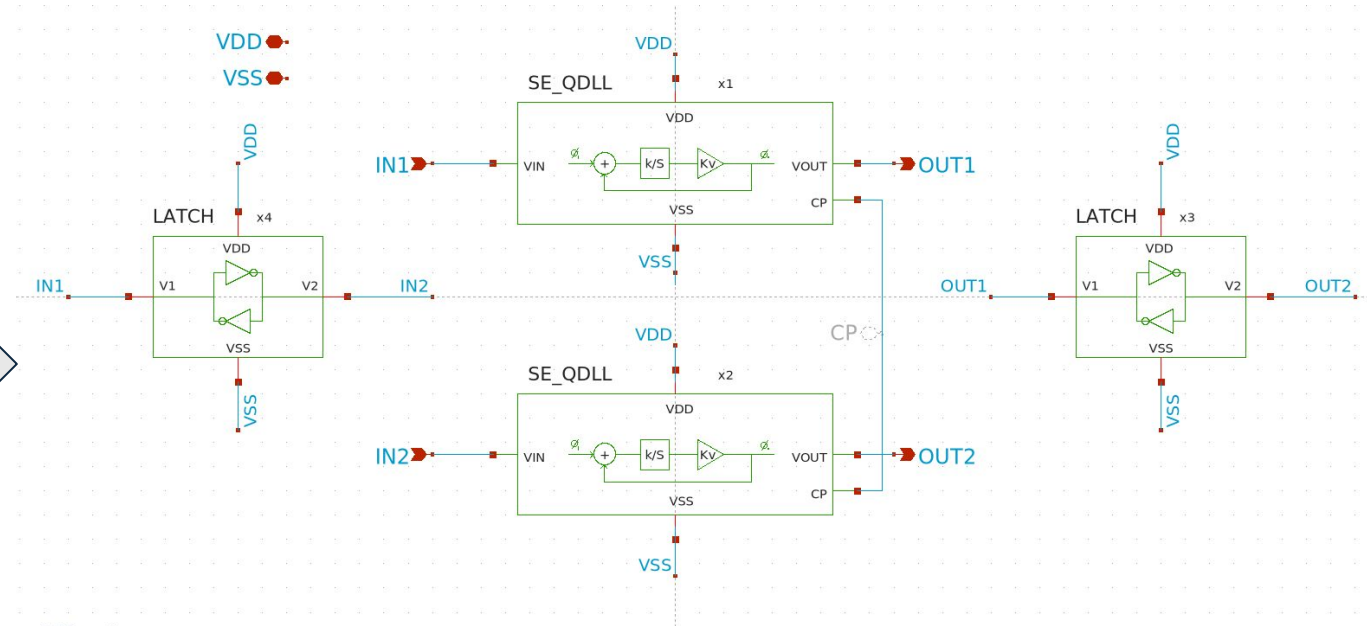

QDLL_TOP.sch

Estimated Number of Pins:*

Input:*

2

Output:*


2

Bidirectional:*


2

3 - QDLL Schematics

- Single-Ended QDLL:

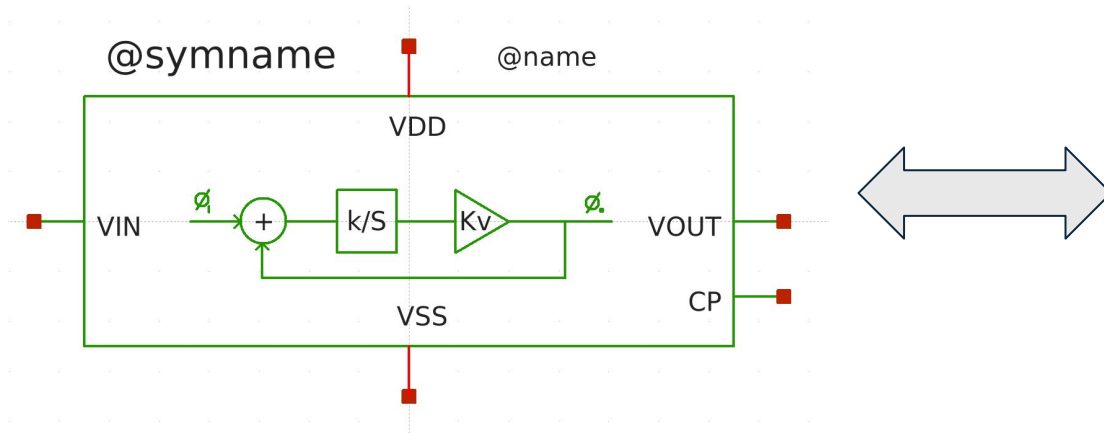


SE_QDLL.sym

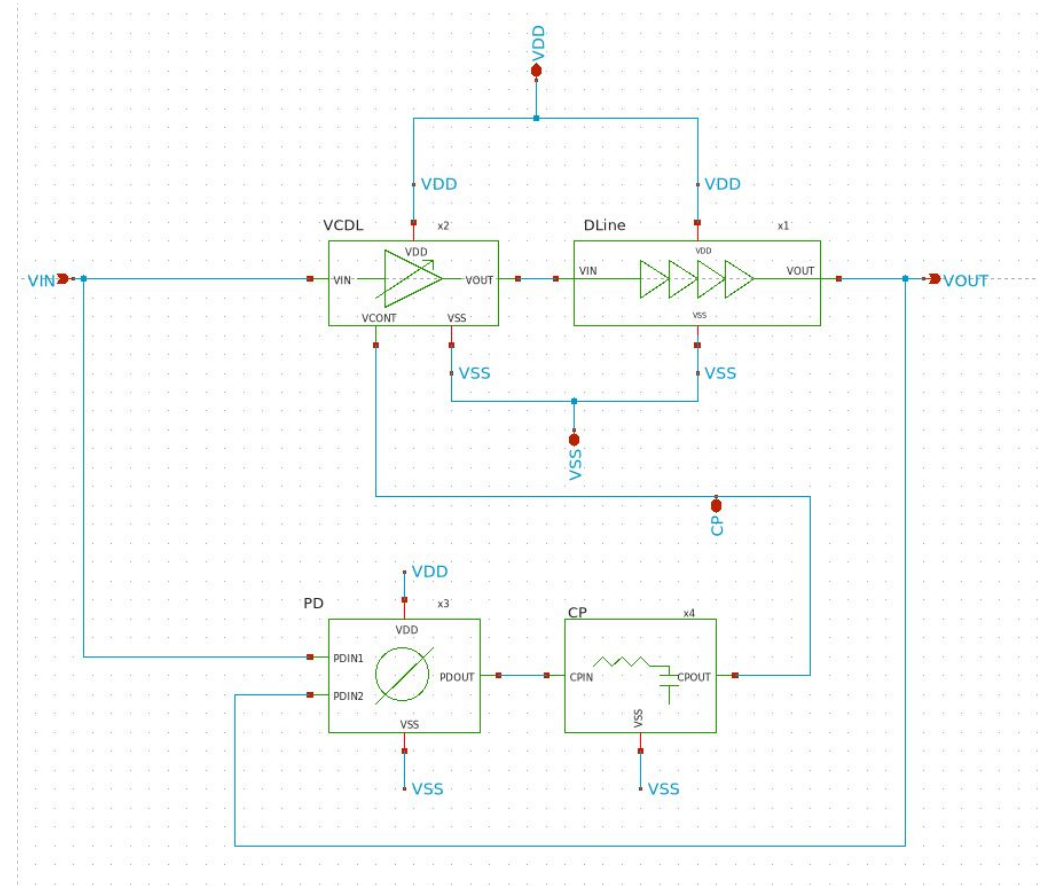


SE_QDLL.sch

3 - QDLL Schematics & Layouts


- Voltage-Controlled Delay Line (VCDL) :

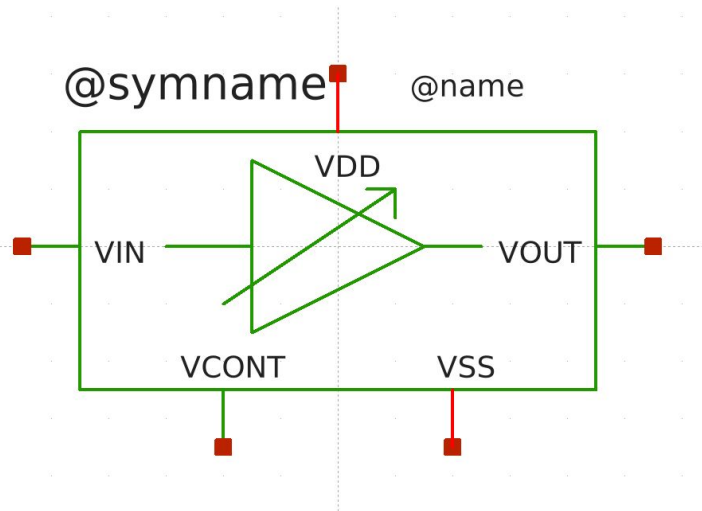

VCDL.sym

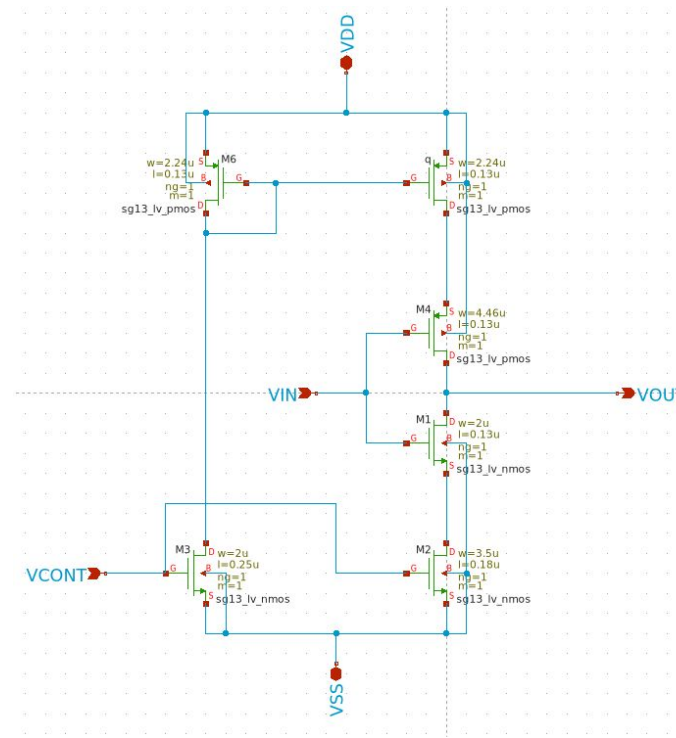

VCDL.sch

 


VCDL Layout



3 - QDLL Schematics & Layouts

- Large delay Line + Buffer Stage (DLine) :

DLine + Buffer Layout

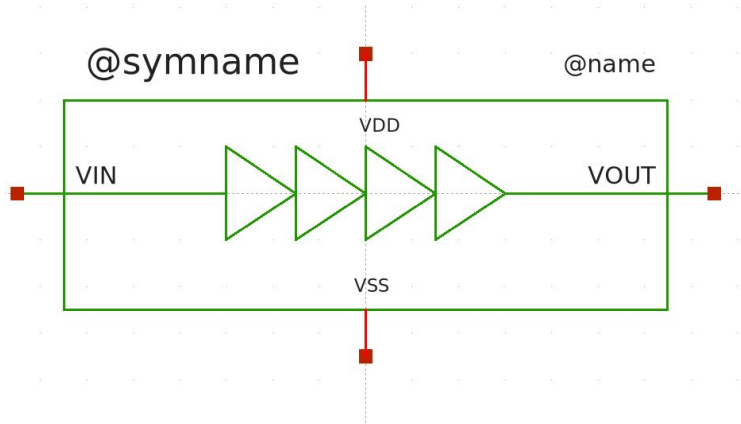


DLine.sym

  


DLine.sch

3 - QDLL Schematics & Layouts


- Phase Detector (XOR cell) :

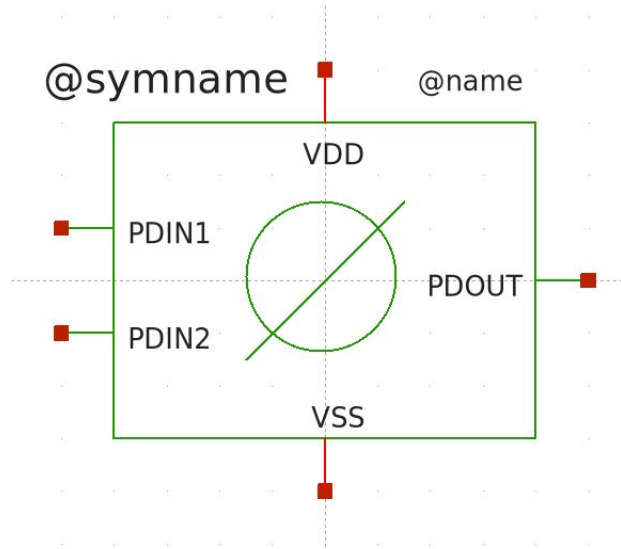

PD.sym

 




PD Layout

 

PD.sch


3 - QDLL Schematics & Layouts

- Charge-Pump/ RC Loop Filter:

   


3 - QDLL Schematics & Layouts


- Series Resistors:

 

RES.sym

 


RES Layout

 


RES.sch

3 - QDLL Schematics


- Flywheel Latches:

 

LATCH.sym

 

LATCH.sch

 


LATCH Layout



4- QDLL Characterization Testbenches

4 - QDLL Testbenchs

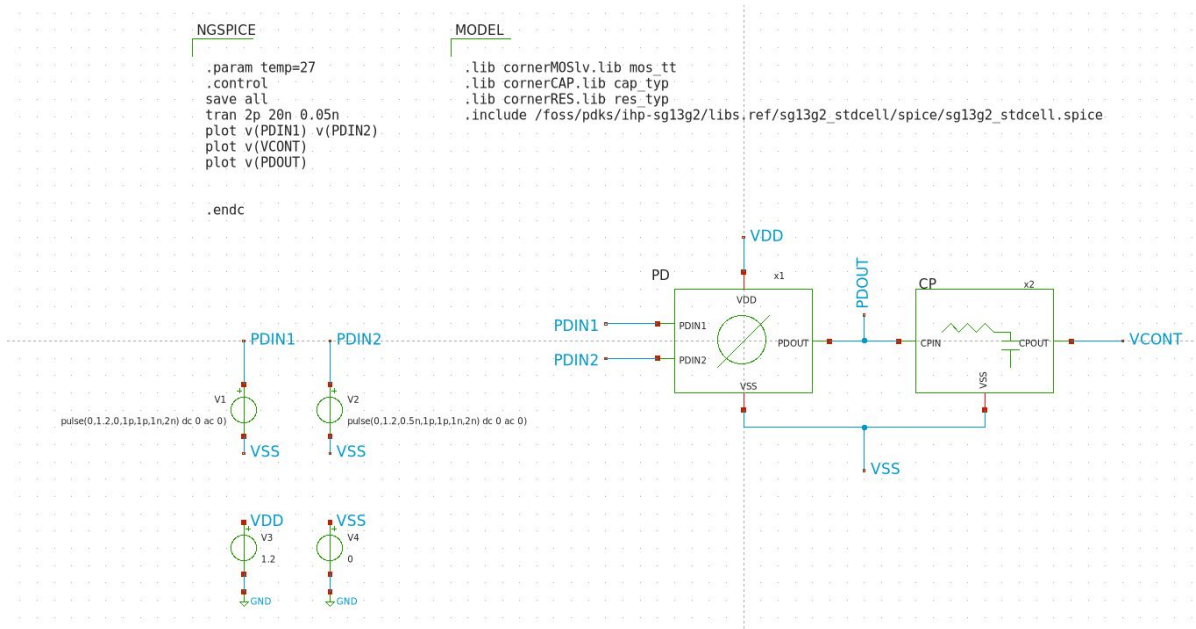- PD + CP Characterization Testbench
 - For Vcont vs Phase Diff Curves




We only use the PD+CP
up to 180°

 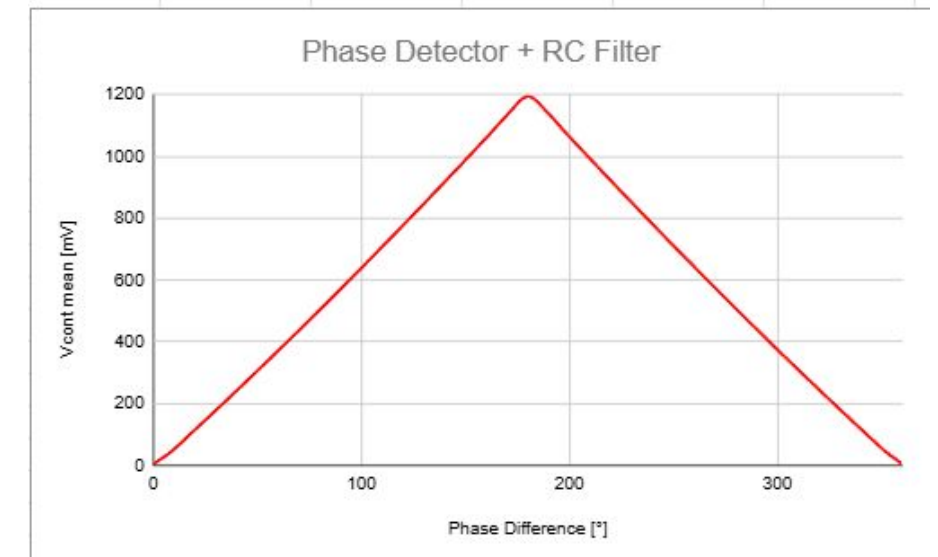


4 - QDLL Testbenchs

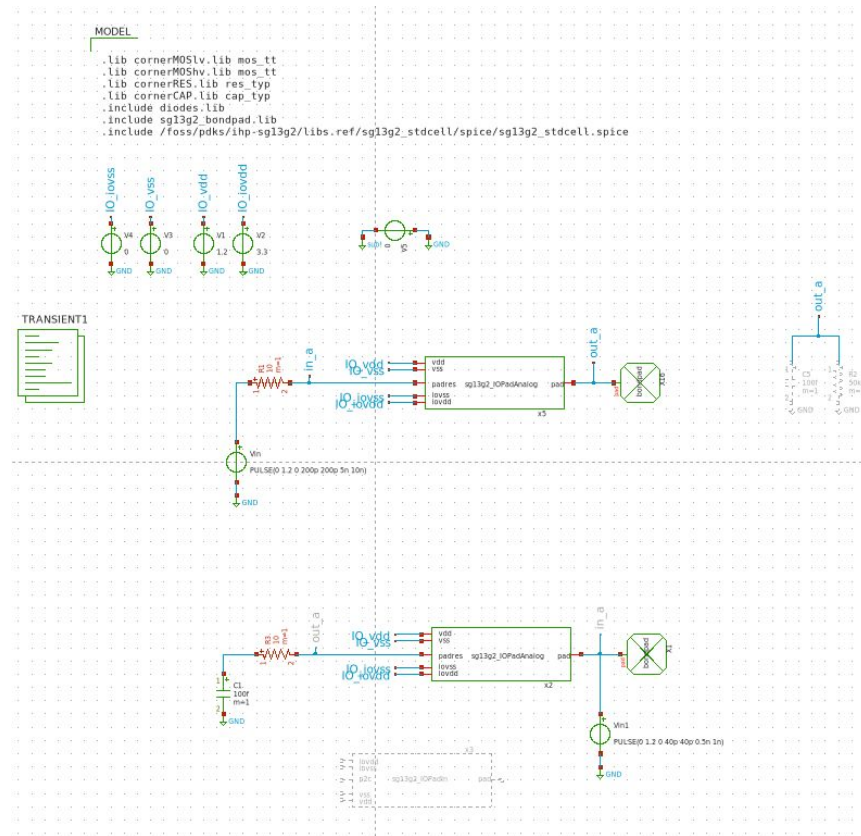- IO CELLS Characterization Testbench
 - For BW delimitation and delay responses




tb_sg13g2_IOPadAnalog.sch

Pad to Pads

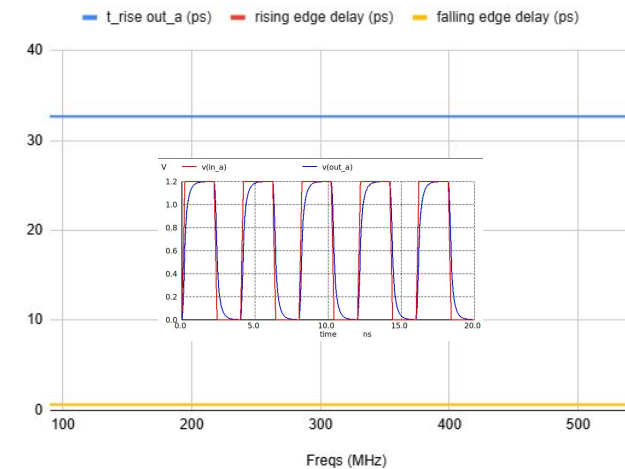


Padres to Pad

 

At 250 MHz the Analog IOCell presents low delay:
padres-to-pad = 37°; pad -to-padres = 3°


4 - QDLL Testbenchs

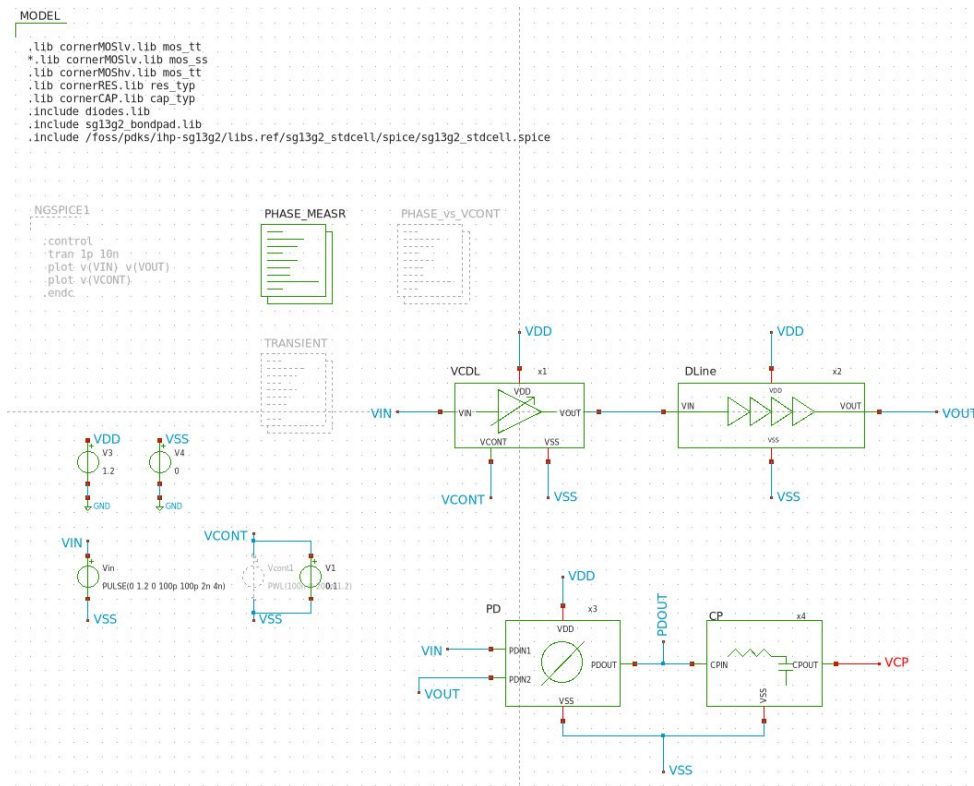- Open Loop for Large Delay Line Characterization Testbench
 - For Phase Diff vs Vcont Curves



tb_open_loop.sch

VCDL vs PD+CP

 

We can adjust the circuit in a way to obtain the desired intercept point → Fixed Phase Difference

5- QDLL TOP Testbench

5 - QDLL TOP Testbench (TT)

- TOP Testbench with the IOCELLS

MODEL

```
.lib cornerMOSlv.lib mos tt
*.lib cornerMOSlv.lib mos ss
.lib cornerMOSlv.lib mos tt
.lib cornerRES.lib res typ
.lib cornerCAP.lib cap typ
.include diodes.lib
.include sg13g2_bondpad.lib
.include /foss/pdks/ihp-sg13g2/libs.ref/sg13g2_stdcell/spice/sg13g2_stdcell.spice
```


TRANSIENT_TT

TRANSIENT_SS


TRANSIENT_FF

PHASE_MEASR

→ load waves Ctrl + left click

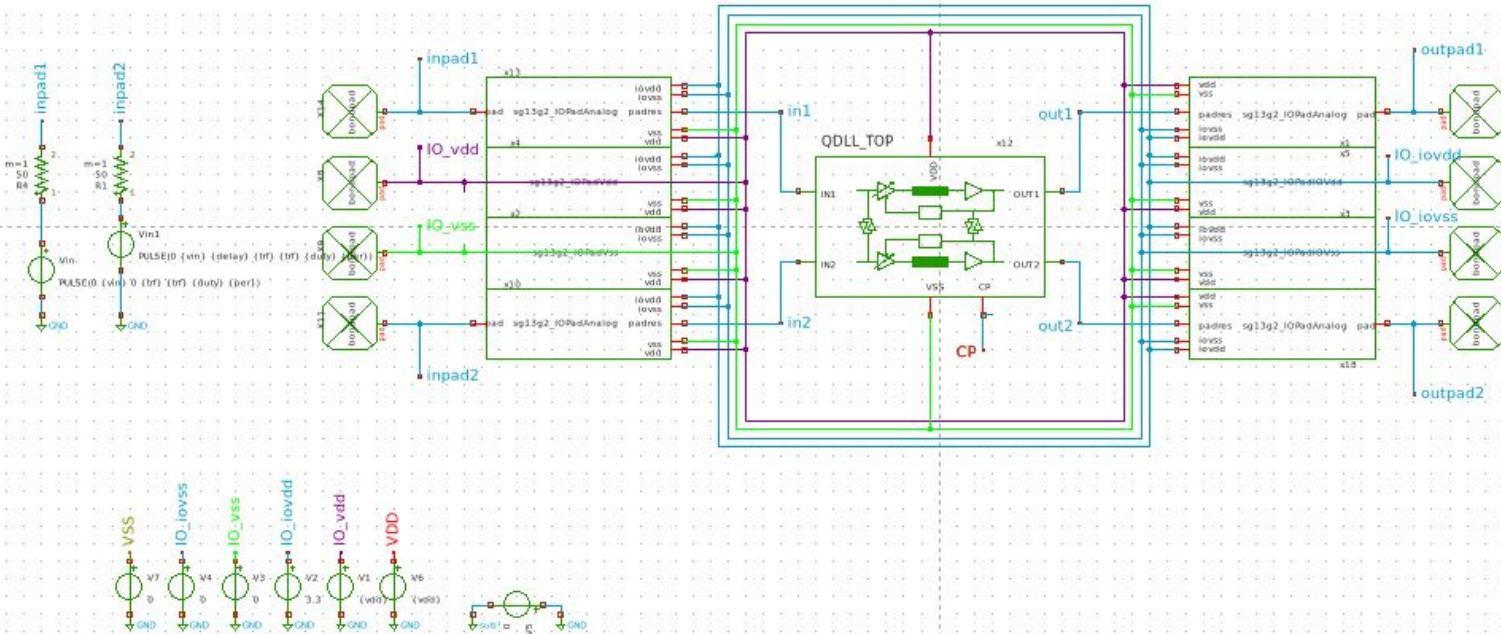


tb_QDLL_TOP.sch

 


5 - QDLL TOP Testbench (TT)

- Setup Time

 

Vcont

 stabilises at approximately 100 ns in 515 mV mean





Python Plot

(You can use phase_analysis_example.ipynb)

5 - QDLL TOP Testbench (TT)

- Input/Output Signals

  


Phase Dllf	v(inpad1)	v(inpad2)	v(outpad1)	v(outpad2)
v(inpad1)	-	180°	90.04°	270.04°
v(inpad2)	180°	-	270.06°	90.06°
v(outpad1)	90.04°	270.04°	-	180°
v(outpad2)	270.06°	90.06°	180°	-

Phase Dllf	Trise	Tfall
v(outpad1)	400 ps	600 ps
v(outpad2)	400 ps	600 ps


5- QDLL Layout TOP

QDLL Top Layout Placement

$h = 111.96\mu\text{m}$

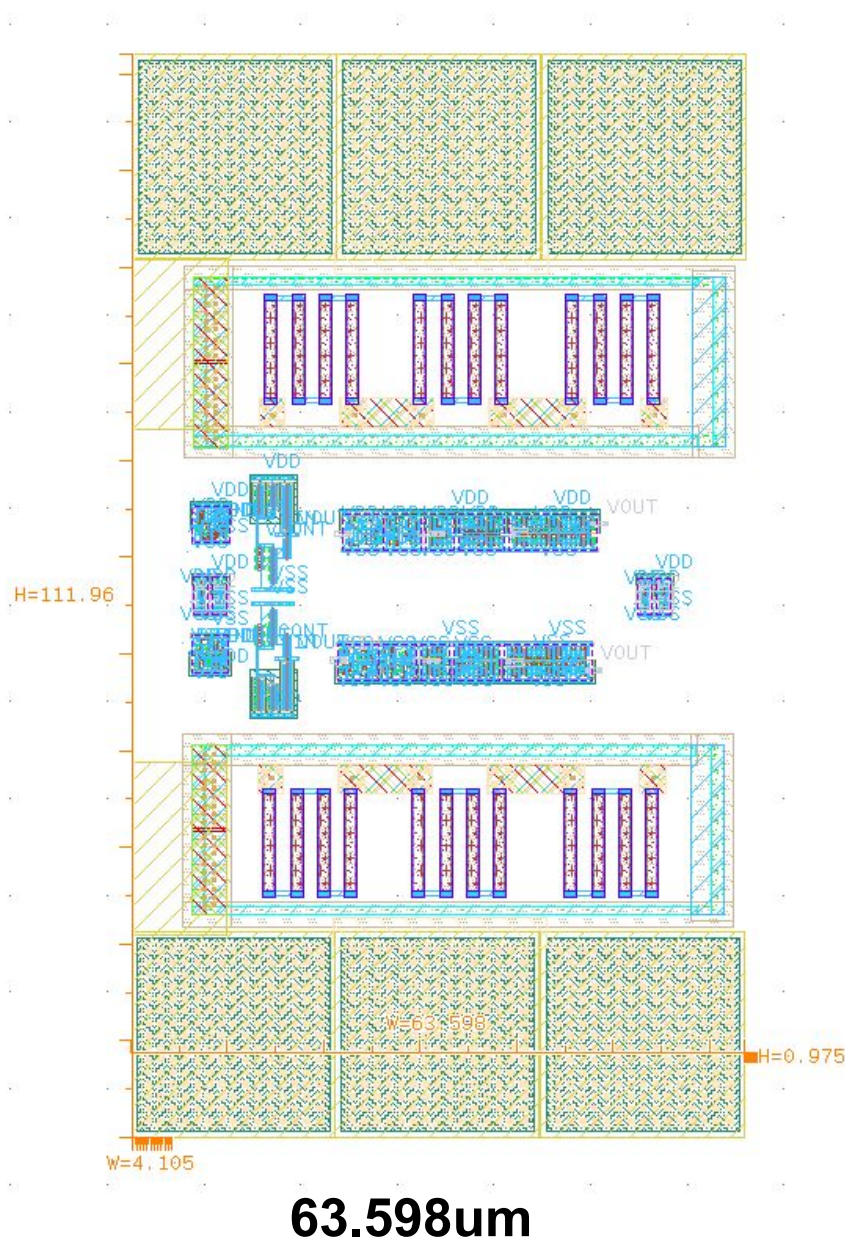


$63.598\mu\text{m}$

 

Vertical View

Area: $111.96\mu\text{m} \times 63.598\mu\text{m} = 7120\mu\text{m}^2 =$


QDLL Top Layout Placement v1

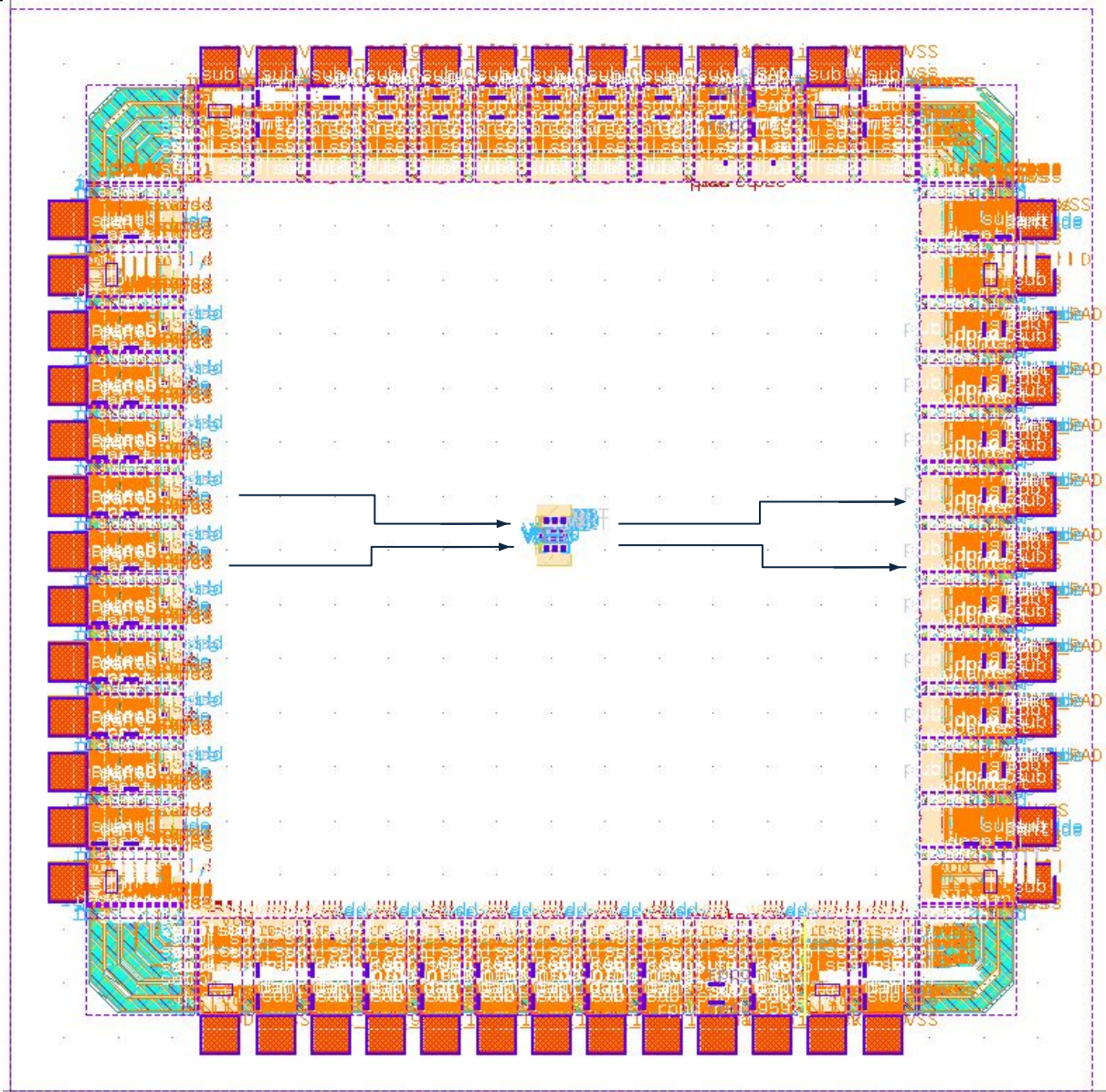

One possible goal would be to place the QDLL vertically and connect the inputs on the left and the outputs on the right with high metal top routing.

For a 250 MHz signal, standard IO cells have been tested and found to perform well. However, if available, we prefer to interface with 50 Ω systems using IO cells with matched impedance.

QDLL layout within the pad ring

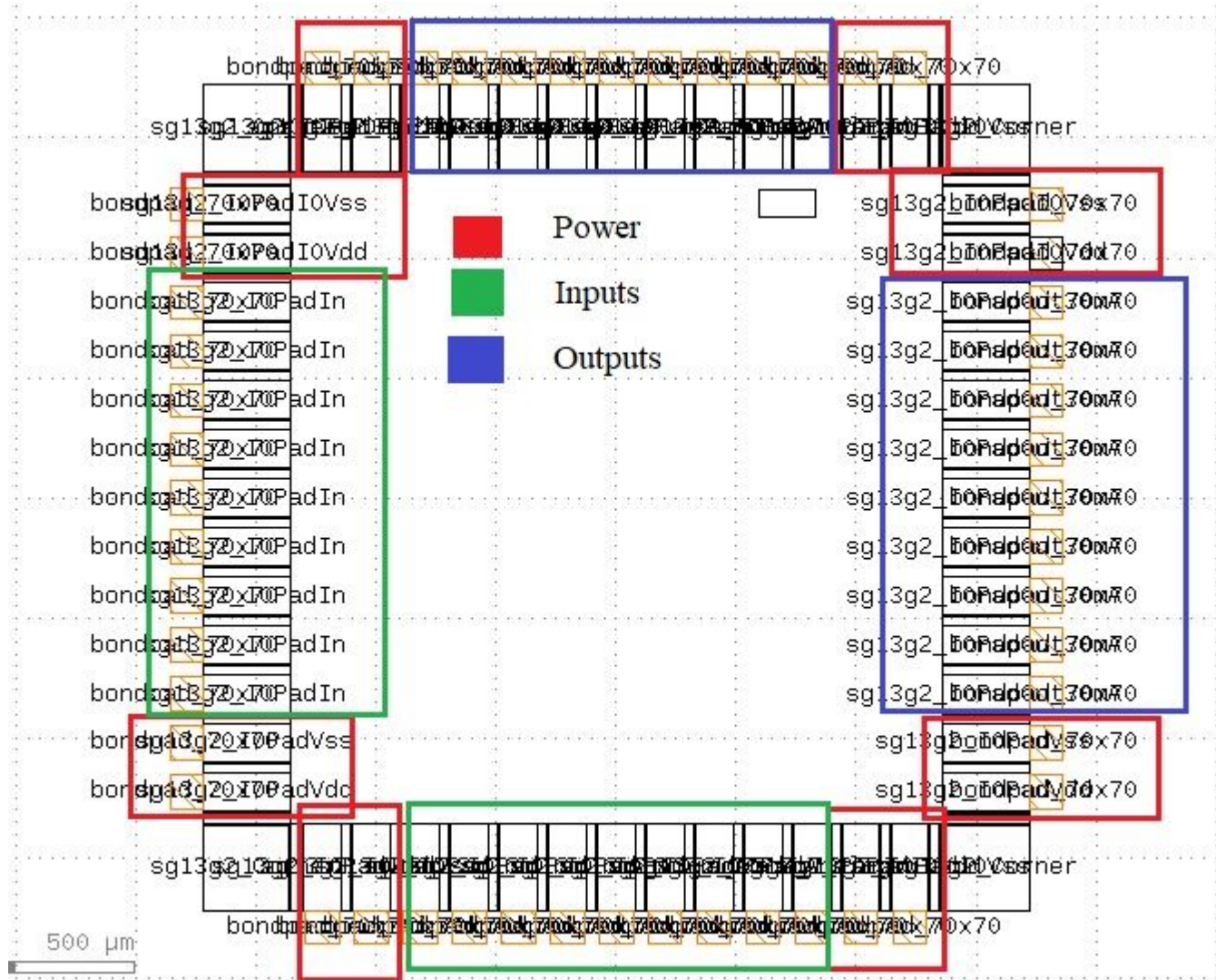



7 - QDLL Pins and IO CELLS

Pins and IO Cells

QDLL Pins

N° Pins: 4

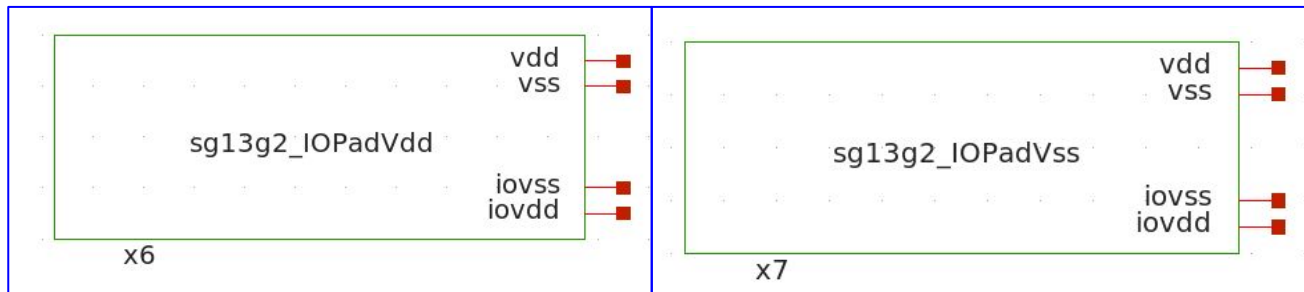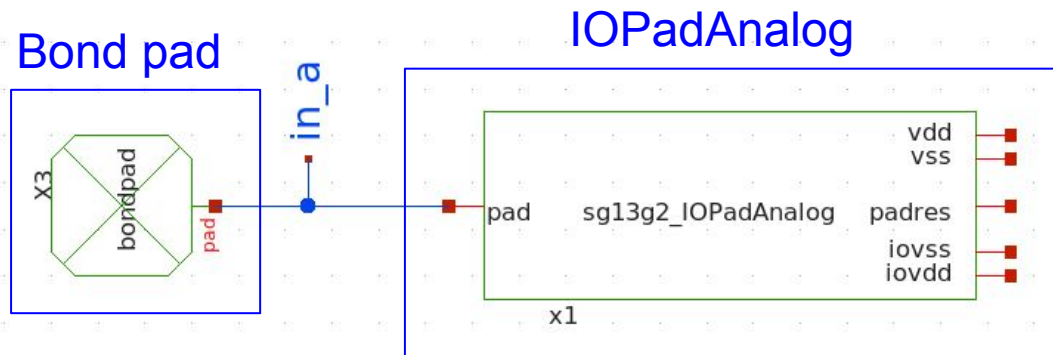- 2 Input Pins
- 2 Output Pin
- 2 Power Supply Pins (VDD , VSS)



Pin Type	Name	IOCELL
Input	inpad1	sg13g2_IOPADAnalog
Input	inpad2	sg13g2_IOPADAnalog
Output	outpad1	sg13g2_IOPADAnalog
Output	outpad1	sg13g2_IOPADAnalog
Power Supply	VDD	sg13g2_IOPadVdd
Power Supply	VSS	sg13g2_IOPadVss

Power Supply IOPads

8- QDLL Project Status

Project Status

Project Status by Block:

TOP	Sub-top	Sub-Block	Symbols & Schematics	Testbench	Prelayout results	IOCELLS results (TT)	IOCELLS results (SS-FF)	Layout (DRC + LVS)	Postlayout results
QDLL TOP	-	-	Done	Done	Done	Done	To do	WIP	To do
-	SE_QDLL	-	Done	Done	Done	Done	To do	WIP	To do
-	-	VCDL	Done	Done	Done	Done	W/P	WIP	To do
-	-	DLine	Done	Done	Done	Done	WIP	Done	To do
-	-	CP	Done	Done	Done	Done	WIP	WIP	To do
-	-	PD	Done	Done	Done	Done	WIP	Done	To do
-	LATCH	-	Done	Done	Done	Done	WIP	Done	To do

We are currently working on the DRC (minimum and maximum) verification of several cells to achieve the desired LVS verification. Next, we plan to compare the extracted views using Magic in order to obtain more realistic results.

On the other hand, multi-corner simulation results are desirable for our project, and we are actively working toward that goal.